

Reg. No.

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

**B.E. / B.TECH DEGREE EXAMINATIONS, MAY 2024**

Second Semester

**CS22202 – DIGITAL PRINCIPLES AND SYSTEM DESIGN***(Common to CS & AD)***(Regulation 2022)****TIME: 3 HOURS****MAX. MARKS: 100**COURSE  
OUTCOMES

STATEMENT

RBT  
LEVEL

<b>CO 1</b>	Students will be able to learn the different types of number systems and simplification of Boolean functions	<b>1</b>
<b>CO 2</b>	Students will be able to understand various logic gates and their usage	<b>2</b>
<b>CO 3</b>	Students will be able to study, analyze and design various combinational circuits and its implementation using VHDL	<b>4</b>
<b>CO 4</b>	Students will be able to understand the different type of memory and their structures	<b>2</b>
<b>CO 5</b>	Students will be able to study, analyze of RTL notation register operations in a clocked sequential circuit	<b>4</b>

**PART- A (20 x 2 = 40 Marks)**

(Answer all Questions)

		CO	RBT LEVEL
<b>1.</b>	Simplify the following Boolean Function $F=X'Y'+XY+X'Y$ .	<b>1</b>	<b>1</b>
<b>2.</b>	What are the limitations of K-map?	<b>1</b>	<b>1</b>
<b>3.</b>	State and Prove Involution law.	<b>1</b>	<b>1</b>
<b>4.</b>	Convert the following Decimal(0.6875) <sub>10</sub> to Binary.	<b>1</b>	<b>1</b>
<b>5.</b>	Define Combinational circuits.	<b>2</b>	<b>2</b>
<b>6.</b>	Write the Truth Table for full adder.	<b>2</b>	<b>2</b>

7.	Write short notes on propagation delay.	2	2
8.	Design a 1-bit magnitude comparator.	2	2
9.	Differentiate between latches and flip flops.	3	3
10.	What is meant by edge triggered flip flops?	3	3
11.	Summarize the characteristic table and equation of JK flip flop.	3	3
12.	What is shift register and Classify its types?	3	3
13.	A seven bit Hamming code is received as 1111110.What is the correct code?	4	2
14.	List the major difference between PLA and PAL.	4	2
15.	What is volatile memory? Give an example.	4	2
16.	How many check bits are required for single bit error detection and correction?	4	2
17.	Discuss briefly about register transfer level.	5	3
18.	Identify the modeling techniques available in HDL.	5	3
19.	Differentiate LOGICAL AND and BITWISE AND operators.	5	3
20.	Define a Sequential Binary multiplier?	5	3

**PART- B (5 x 10 = 50 Marks)**

	Marks	CO	RBT LEVEL
21. (a) (i) Minimize the following expression using Karnaugh Map	(5)	1	1

$$Y=A'BC'D'+A'BC'D+ABC'D'+A'B'CD'$$

(ii) State and Prove Demorgan's theorem (5) 1 1

(OR)


(b) Simplify the following switching functions using Quine McCluskey's tabulation method and realize expression using gates  $F(A,B,C,D) = \Sigma(0,5,7,8,9,10, 11, 14,15)$  (10) 1 1

22. (a) Design and implement a Binary to gray code converter. (10) 2 2

(OR)

(b) Construct a 2 X 4 Encoder and Decoder in detail (10) 2 2

 23. (a) Reduce the number of states in the following State Table. Construct the reduced state table and draw the state diagram. (10) 3 3



(OR)

(b) Design a three bit synchronous counter using JK flip flop. Explain about the execution table and State Table (10) 3 3

24. (a) Implement the following using PAL  $F1(A,B,C)= \Sigma(1,2,4,6)$ ;  $F2(A,B,C) =\Sigma(0,1,6,7)$ ;  $F3(A,B,C)= \Sigma(1,2,3,5,7)$  (10) 4 2

(OR)

(b) Explain about error detection and correction using hamming codes. (10) 4 2

25. (a) Illustrate the HDL operators with their symbol and type of operation performed in RTL. (10) 5 3

(OR)

(b) Illustrate the Algorithmic State Machine chart in detail.

(10) 5 3

**PART- C (1 x 10 = 10 Marks)**

(Q.No.26 is compulsory)

	Marks	CO	RBT LEVEL
26. Construct the following Boolean function using 8:1 multiplexer $F(A,B,C)=\Sigma(1,3,5,6)$ .	(10)	2	2

\*\*\*\*\*