

Reg. No.

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

**B.E./B.TECH. DEGREE EXAMINATIONS, MAY 2024**

Second Semester

**EC22202– CIRCUIT THEORY**

(Electronics and Communication Engineering)

(Regulation 2022)

TIME: 2 HOURS

MAX. MARKS: 60


COURSE OUTCOMES	STATEMENT	RBT LEVEL
CO 1	Apply suitable network theorems and analyze AC and DC circuits.	3
CO 2	Infer the phenomenon of series and parallel resonance in electrical circuits and understand the effect of magnetic coupling between windings.	2
CO 3	Analyze the transient response for any RC, RL and RLC circuits.	4
CO 4	Evaluate the two port network parameters	5
CO 5	Sketch the various network topologies.	4

**PART- A (10 x 2 = 20 Marks)**

(Answer all Questions)


1. Find norton's equivalent resistance ( $R_N$ ) for the below circuit.

CO	RBT LEVEL
1	2

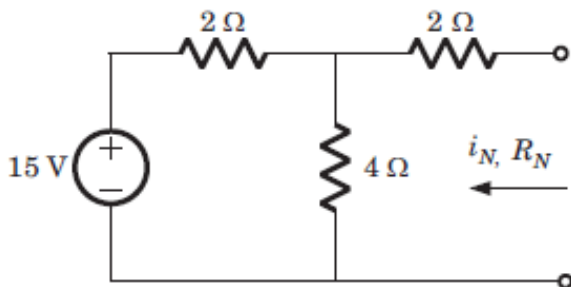

2. Verify the reciprocity theorem for the below circuit.

CO	RBT LEVEL
1	2

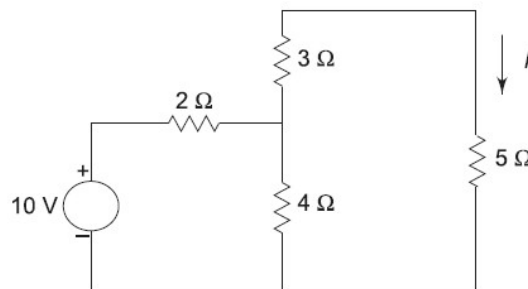



**PART- B (3 x 10 = 30 Marks)**

Marks CO RBT LEVEL


11. (a) A series RLC circuit consists of  $R = 100$  ohms,  $L=0.02$  H and  $C=0.02$  microfarad. Calculate resonance frequency, quality factor, bandwidth, half power frequencies and maximum current at resonance if 100V sinusoidal signal is applied.

(10) 2 4

(OR)


- (b) Find the mesh currents for the circuit shown below,

(10) 2 4

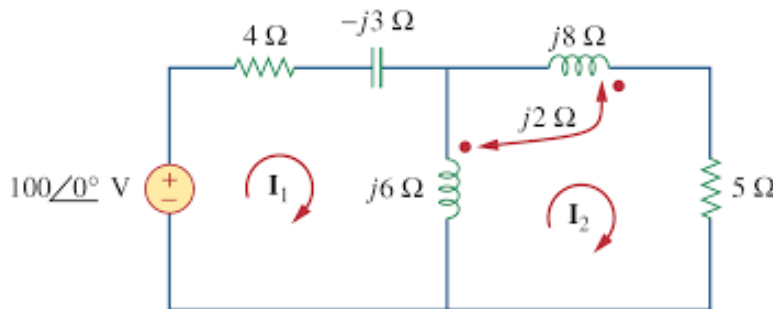

12. (a) The switch in the circuit shown below was in closed position for a long time. Find current  $i_L(t)$  for time  $t > 0$ .


(10) 3 4

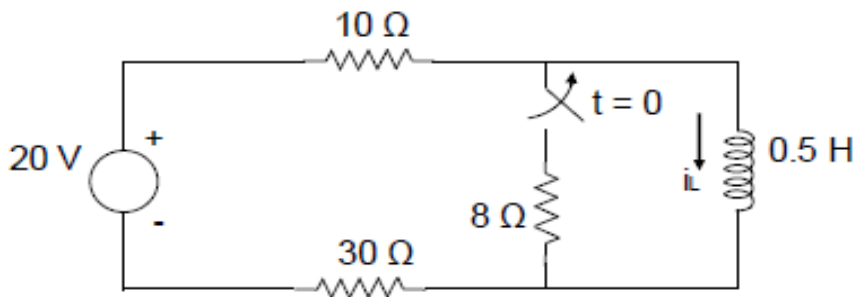


(OR)

- (b) Determine the voltage  $V_C(t)$  and the current  $i_C(t)$  for  $t \geq 0$  for the circuit shown below.

(10) 3 4

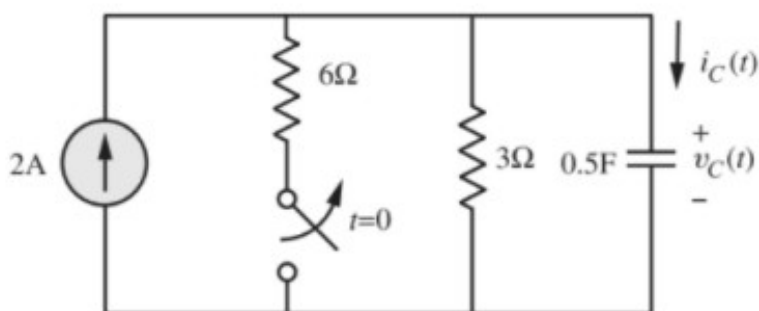


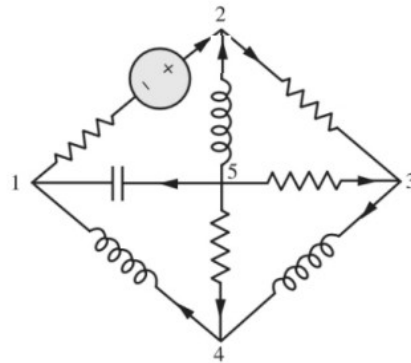13. (a) For the given network, determine the incidence matrix (A), Tie-set matrix (B), and cut-set matrix. (10) 5 4



(OR)

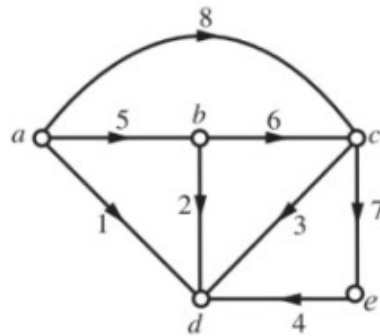
- (b) For the given network graph, determine the incidence matrix (A), Tie-set matrix (B), and cut-set matrix (C). (10) 5 4



**PART- C (1 x 10 = 10 Marks)**  
(Q.No.14 is compulsory)

14. If  $10 \Omega$  resistor is connected across XY terminal as load in the below circuit. Evaluate the current through the  $10 \Omega$  load resistor using thevenin's theorem.

Marks	CO	RBT LEVEL
(10)	1	5

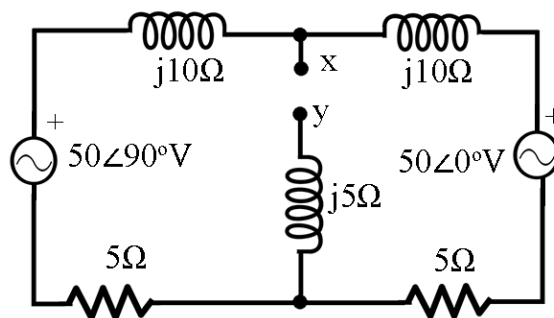

\*\*\*\*\*