

Reg. No.

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

B.E/B.TECH DEGREE EXAMINATIONS, MAY 2024

Third Semester

EC22302 – DIGITAL SYSTEM DESIGN*(Electronics and Communication Engineering)***(Regulation 2022)****TIME: 3 HOURS****MAX. MARKS: 100**

COURSE OUTCOMES	STATEMENT	RBT LEVEL
CO 1	Examine different methods used for simplification of Boolean expressions.	2
CO 2	Design combinational logic circuits using logic gates.	3
CO 3	Design sequential logic circuits using flipflops.	3
CO 4	Investigate and design synchronous and asynchronous sequential circuits.	4
CO 5	Apply the digital circuits for solving real world problems and implement the logic function using different types of PLD.	4

PART- A (20x2=40Marks)


(Answer all Questions)

	CO	RBT LEVEL
1. Simplify $F(A, B) = A^1B + AB + AB^1$.	1	2
2. Express $F = Y + XZ$ in canonical SOP.	1	2
3. Implement using NOR gates only, $F = AB + A^1B^1$.	1	2
4. What is Principle of Duality?	1	2
5. Draw the logic diagram of Half Adder and write its sum and carry expression.	2	2
6. What is barrel shifter?	2	2
7. Compare demultiplexer and decoder.	2	3
8. What is priority encoder?	2	2
9. Write the characteristic equation of JK and D flip flop.	3	2
10. Convert T flip flop to D flip flop.	3	2
11. Differentiate Synchronous and Asynchronous counter.	3	3
12. How many flip flop's are required to build a binary counter that counts from 0 to 511?	3	2
13. Compare Mealy and Moore Machines.	4	3
14. Define state diagram.	4	2
15. Define Race condition.	4	2
16. What are Hazards?	4	2
17. What is the binary value for 14? Express this in to gray code.	5	3
18. Draw the logic circuit of a 1-bit comparator.	5	2

- | | | | |
|------------|---|----------|----------|
| 19. | List the advantages of PLD's. | 5 | 2 |
| 20. | What are the advantages of pipelined adder? | 5 | 2 |

PART- B (5x10=50Marks)

- | | | Marks | CO | RBT LEVEL |
|----------------|---|--------------|----------|-----------|
| 21. (a) | Minimize the following function using K-map.
$F(A, B, C, D, E) = \sum m(0, 5, 6, 8, 9, 10, 11, 16, 20, 24, 25, 26, 27)$ | (10) | 1 | 3 |
| | (OR) | | | |
| (b) | Implement AND, OR, NOT and NOR gate using only NAND gate. | (10) | 1 | 3 |
| 22. (a) | Design a BCD adder and explain its working with necessary block diagram. | (10) | 2 | 3 |
| | (OR) | | | |
| (b) | Explain the operation of a 8 X 1 Multiplexer and Implement the following function using a suitable Multiplexer.
$F(A, B, C, D) = \sum m(0, 1, 3, 5, 6, 7, 8, 9, 11, 13, 14)$ | (10) | 2 | 3 |
| 23. (a) | (i) Convert JK flip flop in to D flip flop.
(ii) Convert T flip flop in to JK flip flop. | (5+5) | 3 | 3 |
| | (OR) | | | |
| (b) | Design a synchronous counter to count the sequence 0, 4, 2, 1, 6, 0, using JK flip flop. | (10) | 3 | 3 |
| 24. (a) | Design a synchronous sequential logic circuit using D flip flops for the following state diagram. Use state reduction if possible. | (10) | 4 | 3 |

 

(OR)

- (b) Design a Mealy machine for a binary input sequence such that if it has a substring 101, the machine output A, if the input has substring 110, it outputs B otherwise it outputs C. (10) 4 3
25. (a) Design a 4-bit binary to gray code converter and draw its logic diagram. (10) 5 3
- (OR)**
- (b) Design a sequence detector which detects the sequence “01110” (with one bit overlapping) using D flip-flop. (10) 5 3

PART- C (1x 10=10Marks)
(Q.No.26 is compulsory)

- | | Marks | CO | RBT LEVEL |
|--|-------|----|-----------|
| 26. Implement a full adder with two 4 x1 Multiplexers. | (10) | 2 | 4 |
