

Reg. No.

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

B.E. / B.TECH. DEGREE EXAMINATIONS, MAY 2024

Fourth Semester

EC22401 – ANALOG INTEGRATED CIRCUITS AND ITS APPLICATIONS*(Electronics and Communication Engineering)***(Regulation 2022)****TIME: 3 HOURS****MAX. MARKS: 100**

COURSE OUTCOMES	STATEMENT	RBT LEVEL
CO 1	Infer the DC and AC characteristics of operational amplifiers and its effect on output and their compensation techniques.	2
CO 2	Elucidate and analyze the linear and non-linear applications of an opamp.	4
CO 3	Classify and comprehend the working principle of data converters.	4
CO 4	Illustrate the function of application specific ICs such as Analog multiplier, PLL and its application in communication.	2
CO 5	Explain the working of multivibrators using IC 555, the special function ICs such as Voltage regulators, buck-boost converters, A/V amplifiers etc.	3

PART- A (20 x 2 = 40 Marks)

(Answer all Questions)

	CO	RBT LEVEL
1. List the assumptions to be made for op-amp analysis.	1	2
2. Define CMRR. Justify why CMRR should be high for op-amp.	1	3
3. Draw the circuit diagram of the Voltage follower and output waveform if the input is a sinusoidal signal.	1	2
4. Explain the virtual ground concept in op-amp.	1	2
5. Mention two linear and two non-linear applications of an op-amp.	2	2
6. Illustrate how a differential amplifier using op-amp can be converted into a subtractor circuit.	2	3
7. Point out the need for converting a first order filter into a higher order filter.	2	3
8. Sketch the circuit diagram of antilog amplifier using an op-amp.	2	2

9.	Show the block diagram of sample and hold circuit.	3	2
10.	List out the specifications of DAC.	3	2
11.	State the advantages of R-2R ladder DAC over binary weighted type DAC.	3	2
12.	Obtain the number of comparators required for realizing a 4-bit flash ADC.	3	3
13.	Summarize the basic analog multiplication techniques.	4	2
14.	Give the limitations of emitter coupled transistor pair analog multiplier.	4	2
15.	State the various applications of PLL.	4	2
16.	Interpret the relation between capture range and lock range in a PLL.	4	3
17.	Justify the need for voltage regulator ICs.	5	3
18.	Draw the functional block diagram of IC 723 regulator.	5	2
19.	List the characteristics and applications of Optocoupler.	5	2
20.	Analyze the purpose of one shot multivibrator.	5	2

PART- B (5 x 10 = 50 Marks)

		Marks	CO	RBT LEVEL
21. (a)	Construct the BJT differential amplifier and explain its operation. Derive the expression for CMRR.	(10)	1	3
	(OR)			
(b)	List and explain the DC characteristics of an operational amplifier.	(10)	1	3
22. (a)	With a suitable circuit diagram, explain the operating principle of an instrumentation amplifier and derive its gain.	(10)	2	4
	(OR)			
(b)	(i) Analyse the first order Low pass filter and derive its voltage gain.	(6)	2	4
	(ii) Design a first order low pass Butterworth filter using operational	(4)	2	4

amplifier for the upper cut off frequency of 2.5kHz. Assume the value of capacitor to be 0.1 μ F.

- | | | | | |
|----------------|---|-------------|----------|----------|
| 23. (a) | Analyze the working of R-2R ladder type DAC. | (10) | 3 | 3 |
| | (OR) | | | |
| (b) | (i) Describe about the Successive approximation type ADC with neat sketch. | (6) | 3 | 3 |
| | (ii) Show the conversion sequence using Successive approximation type ADC for an input of 110110110110 . | (4) | 3 | 3 |
| 24. (a) | Analyze the Gilbert's multiplier cell with a neat circuit diagram. | (10) | 4 | 3 |
| | (OR) | | | |
| (b) | Illustrate the operation of VCO with block diagram. Derive the expression for f_0 and voltage to frequency conversion factor. | (10) | 4 | 3 |
| 25. (a) | Explain the working of Astable Multivibrator. List applications in detail. | (10) | 5 | 3 |
| | (OR) | | | |
| (b) | (i) Discuss in detail the working principle of switching regulator. | (6) | 5 | 3 |
| | (ii) Examine the operation of frequency to voltage converters. | (4) | 5 | 3 |

PART- C (1 x 10 = 10 Marks)

(Q.No.26 is compulsory)

- | | | Marks | CO | RBT
LEVEL |
|------------|--|-------------|----------|--------------|
| 26. | Design a practical integrator circuit with a D.C. gain of 10 to integrate a square wave of 10 kHz. | (10) | 2 | 5 |
