

Reg. No.

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

B.E. / B.TECH. DEGREE EXAMINATIONS, MAY 2024

First Semester

EE18153 – ELECTRICAL MACHINES AND DRIVES*(Chemical Engineering)***(Regulation 2018/2018A)****TIME: 3 HOURS****MAX. MARKS: 100**

COURSE OUTCOMES	STATEMENT	RBT LEVEL
CO 1	Apply basic electrical laws for the electrical circuits and understand working of various measuring instruments.	3
CO 2	Analyze the characteristics of various semiconductor devices and develop circuits for an application.	4
CO 3	Analyze and select electrical machines for drive applications based on characteristics.	5
CO 4	Identify the structure and types of Electrical drives for specific applications.	3
CO 5	Apply AC-DC, DC-DC, DC-AC and AC-AC converter control methods for Electrical Machine and Drives.	3

PART- A (10 x 2 = 20 Marks)

(Answer all Questions)

	CO	RBT LEVEL
1. Classify different types of measuring instruments used.	1	2
2. A pure inductive coil allows a current of 10A to flow from a 200V, 50Hz supply. Find inductance of the coil.	1	3
3. Sketch the single phase bridge converter with RLE load.	2	2
4. Compare ripple factor of half wave and full wave rectifier circuit.	2	2
5. Justify the purpose of using starter for motor.	3	5
6. Illustrate the torque-slip characteristics of three phase induction motor.	3	3
7. List the basic elements of electrical drives.	4	1
8. Compare AC Drives with DC Drives.	4	3
9. List the various conventional speed controls employed for DC motor.	5	1
10. What do you mean by VVVF control and mention its advantages?	5	1


PART- B (5 x 14 = 70 Marks)

	Marks	CO	RBT LEVEL
11. (a) With simple sketch explain on different types of Torques used in Analog Measuring instruments.	(14)	1	3

(OR)

(b) Determine the mesh current for the following electrical network

(14) 1 3

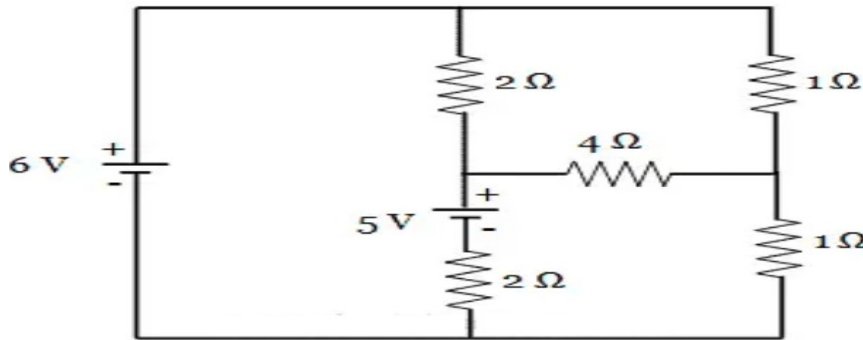

12. (a) With neat sketch, explain the static VI characteristics of SCR. (14) 2 3

(OR)

(b) Explain the operation of three phase semi converter circuit with R load. (14) 2 3

13. (a) Explain the working principle of three point starter used for DC Shunt motor with neat diagram. (14) 3 4

(OR)

(b) (i) Explain the various braking methods used for Induction motor. (8) 3 4

(ii) Explain the operation of three phase auto transformer starter. (6) 3 4

14. (a) (i) Summarize the factors influencing the choice of electrical drives. (6) 4 2

(ii) Paraphrasing various types of electrical drives with neat diagram. (8) 4 2

(OR)

(b) Summarize the classes of duty. With the help of load verses time diagram explain various classes of duties. (14) 4 2

15. (a) Classify the DC to DC converters. Explain the four quadrant chopper with neat diagram. (14) 5 3

(OR)

(b) With neat circuit configuration explain the modes of operation of static Kramer method of slip power recovery system for SRIM. (14) 5 3

PART- C (1 x 10 = 10 Marks)

(Q.No.16 is compulsory)

	Marks	CO	RBT LEVEL
16. Reviewing the operation of three phase AC voltage controller circuit.	(10)	5	5
