

Reg. No.

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

B.E./ B.TECH. DEGREE EXAMINATIONS, MAY 2024

Third Semester

EE18301 – ELECTRON DEVICES AND CIRCUITS*(Electrical and Electronics Engineering)***(Regulation 2018/2018A)****TIME:3 HOURS****MAX. MARKS: 100**

COURSE OUTCOMES	STATEMENT	RBT LEVEL
CO 1	Describe and analyse different types of PN devices.	4
CO 2	Describe and analyse different types of current and Voltage controlled devices	4
CO 3	Analyse performance of devices using small signal model	4
CO 4	Design and implementation of various electronic devices in circuits	4

PART- A(10x2=20Marks)

(Answer all Questions)

		CO	RBT LEVEL
1.	Relate the voltage and current of forward biased pn junction diode.	1	3
2.	What are the limitations of Zener diode regulator?	1	2
3.	State the operating modes of BJT with reference to junction biasing	2	2
4.	How ac equivalent circuit is obtained in BJT amplifier?	3	3
5.	Why thermal runaway is not occur in FETs?	2	2
6.	Draw the high frequency equivalent circuit for the MOSFET.	3	2
7.	State the need for neutralization in tuned amplifiers.	4	2
8.	An amplifier has a midband gain of 100 and has a bandwidth of 200KHz. Find the bandwidth, when negative feedback is applied with feedback ratio of 0.04.	4	3
9.	List out the disadvantages of RC phase shift oscillator.	4	2
10.	Mention the applications of Opto-coupler.	4	2

PART- B (5x 14=70Marks)

		Marks	CO	RBT LEVEL
11. (a)	With the neat circuit diagram and waveform, explain the operation of a half wave rectifier which produces a positive output voltage. Also derives its various parameters.	(14)	1	3
(OR)				
(b)	(i) Enumerate the concept of Zener breakdown in PN junction with its V-I Characteristics.	(7)	1	3
	(ii) With the neat circuit diagram and waveform, describe the operation of biased parallel clipper.	(7)	1	3
12. (a)	From the two port model of BJT amplifier in CE configuration, Derive the expression for input impedance, current gain voltage gain and output	(14)	3	3

impedance.

(OR)

- (b) Derive the expression for current gain, voltage gain, input impedance and output impedance for an emitter follower circuit. (14) 3 3
13. (a) (i) In a certain application needs the voltage controlled resistor component. Identify and explain the characteristics of that component. (8) 2 3
 (ii) The data sheet of an enhancement MOSFET gives $I_{D(on)}=400\text{mA}$ at $V_{GS}=10\text{V}$ and $V_{GS(th)}=1\text{V}$. Find the drain current for $V_{GS}=5\text{V}$. (6) 2 3
- (OR)
- (b) With neat diagram, Illustrate the operation and characteristics of normally on MOSFET. (14) 2 3
14. (a) Illustrate the operation of emitter coupled differential amplifier and deduce the expression for common mode and differential mode gains. (14) 4 3
- (OR)
- (b) Identify the feedback topology used in Common emitter amplifier circuit with emitter resistance and derive the voltage gain, input impedance and output impedance with feedback. (14) 4 3
15. (a) Discuss the principle and operation of a Hartely oscillator with a circuit. Also deduce an expression for frequency of oscillations. (14) 4 3
- (OR)
- (b) (i) Analyze the operation of a twisted – nematic field-effect LCD in its transmissive and reflective mode operation (10) 4 3
 (ii) Compare the LED with pn junction diode. (4) 4 3

PART- C (1x 10=10Marks)

(Q.No.16 is compulsory)

- | | Marks | CO | RBT LEVEL |
|--|-------|----|-----------|
| 16. For the circuit shown in figure below, $V_{CC}=20\text{V}$, $R_C=2\text{K}\Omega$, $\beta=50$, $V_{BE}=0.2\text{V}$, $R_1=100\text{K}\Omega$, $R_2=10\text{K}\Omega$, $R_E=100\Omega$. Calculate I_B , V_{CE} , I_C and Stability factor. | (10) | 2 | 4 |


