

Reg. No.

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

B.E./ B.TECH. DEGREE EXAMINATIONS, MAY 2024

Fifth Semester

EE18502 – POWER ELECTRONICS*(Electrical and Electronics Engineering)***(Regulation 2018/ 2018A)****TIME:3 HOURS****MAX. MARKS: 100**

COURSE OUTCOMES	STATEMENT		RBT LEVEL
CO 1	Acquire knowledge about fundamental concepts and techniques used in Power Electronics.		4
CO 2	Ability to identify basic requirements for Power Electronics based design applications.		4
CO 3	Develop skills to build and troubleshoot Power Electronics circuits.		4
CO 4	Ability to understand the use of Power Converters in Commercial and Industrial applications.		4

PART- A (10x2=20Marks)

(Answer all Questions)

		CO	RBT LEVEL
1.	Differentiate holding current from latching current.	1	2
2.	What is the purpose of using snubber circuit?	1	2
3.	Classify the different types of controlled rectifier.	1	3
4.	Write the relation between firing angle and extinction angle in single phase fully controlled rectifier when operating with RL load.	1	3
5.	A step down chopper has input voltage of 200 V with 10 Ω load resistor connected, voltage drop across chopper is 2 V when it is ON, For a duty cycle of 0.6 calculate the average output voltage?	2	3
6.	Name the three types of control strategies available for DC choppers.	2	2
7.	Contrast voltage source and current source inverters.	3	4
8.	A single phase half bridge inverter feeds resistive load of 5 Ω . When supply voltage of 120V, determine the fundamental component of RMS output voltage.	3	4
9.	Compare integral cycle control and phase control in AC voltage controllers.	4	2
10.	Sketch the matrix converter and mention its advantages.	4	2

PART- B (5x 14=70Marks)

		Marks	CO	RBT LEVEL
11. (a)	Illustrate the structure and different modes of operation with the characteristics of MOSFET.	(14)	1	3
(OR)				
(b)	(i) Describe the various types of turn ON methods in SCR.	(7)	1	3

- (ii) Draw the two-transistor model of SCR and derive an expression for anode current. (7) 1 3
12. (a) Describe the working of single phase fully controlled bridge converter in the Rectifying mode and inversion mode. And derive the expressions for average output voltage and rms output voltage. (14) 1 4
(OR)
- (b) Interpret the effect of Source Inductance on the performance of single-phase fully controlled converter and derive the expression for output voltage. (14) 1 4
13. (a) A DC chopper has an input voltage of 200 V and a load of 8Ω resistance. The voltage drop across thyristor is 2 V and the chopping frequency is 800 Hz. The duty cycle of 0.5, Calculate a) Average output voltage b) RMS output voltage c) Chopper efficiency and d) Input resistance. (14) 2 3
(OR)
- (b) Derive the expression for voltage gain in a DC-DC boost converter and explain the different modes of operation with relevant waveforms. (14) 2 3
14. (a) With neat sketches, explore the operation of three phase voltage source inverter. Draw phase and line voltage waveforms on the assumption that each thyristor conducts for 180° and the resistive load is star connected. (14) 3 4
(OR)
- (b) Categorize techniques used to reduce the harmonics content in the inverter and with relevant diagram, explain about any two of them. (14) 3 4
15. (a) (i) Illustrate the working of single phase half wave A.C voltage regulator with R load using voltage and current waveform and derive its average output voltage and power factor. (7) 4 3
(ii) A single phase voltage controller has input voltage of 230 V, 50 Hz and a load of 15Ω resistance for 6 cycles ON and 4 cycles OFF. Calculate (a) RMS output voltage, (b) input power factor (c) Average and RMS thyristor currents. (7) 4 3
(OR)
- (b) With neat sketch and relevant waveforms, explain the working of single phase to single phase step-up cycloconverter with resistive load. (14) 4 3

PART- C (1x 10=10Marks)

(Q.No.16 is compulsory)

- | | | Marks | CO | RBT
LEVEL |
|-----|--|-------|----|--------------|
| 16. | Construct the circuit to obtain DC output voltage from a single phase AC input supply using two thyristors and two diodes should be connected in symmetrical configuration and derive the expression for RMS and average output voltage. | (10) | 2 | 5 |