

Reg. No.

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

B.E./ B.TECH. DEGREE EXAMINATIONS, MAY 2024

First Semester

EE22151– BASIC ELECTRICAL AND ELECTRONICS ENGINEERING*(Common to all branches except CH, EE, EC)***(Regulation2022)****TIME:3 HOURS****MAX. MARKS: 100**


COURSE OUTCOMES	STATEMENT	RBT LEVEL
CO 1	Compute the electric circuit parameters for simple problems	4
CO 2	Understand the construction and characteristics of different electrical machines.	4
CO 3	Describe the fundamental behavior of different semiconductor devices and circuits.	4
CO 4	Design basic digital circuits using Logic Gates and Flip-Flops.	4
CO 5	Analyze the operating principle and working of measuring instruments.	4

PART- A(20X2=40Marks)*(Answer all Questions)*

	CO	RBT LEVEL
1. Two resistors of 5 Ω and 9 Ω are connected in parallel and a voltage of 200 V is applied to the terminals .Find the total current taken by the circuit.	1	3
2. In a closed loop of resistors the algebraic sum of the electro motive forces is 10 V. What is the voltage drop across the resistors in that loop? Assume R=10 Ω , I=1A.	1	4
3. For the pure resistive circuit excited by sinusoidal varying voltage, what are the phase angle and power factor?	1	4
4. State the relation between line & phase quantities of a balanced 3 phase star connected system.	1	3
5. What is the purpose of yoke in a DC machine?	2	3
6. What is the significance of back EMF in DC motor?	2	3
7. State the applications of a DC motor.	2	2
8. In a single phase transformer, $N_p = 350$ turns, $N_s = 1050$ turns, $E_p = 400V$. Find E_s .	2	3
9. Write the difference between PN junction diode and Zener diode.	3	3
10. List the advantages of bridge rectifier.	3	2
11. Draw the energy band structure of a semiconductor.	3	2
12. Why Common Emitter configuration is used in amplifier circuits?	3	4
13. Define half adder.	4	2
14. Tell the basic applications of flip flop.	4	2
15. Name the problem associated with the asynchronous counter.	4	4
16. List out the classification of sequential circuits.	4	2
17. What are absolute instruments?	5	2
18. What is the purpose of registering mechanism?.	5	3
19. Name the types of instruments used for making voltmeter and ammeter..	5	3
20. Write down the deflecting torque equation in dynamometer type wattmeter.	5	3

PART- B (5x 10=50Marks)

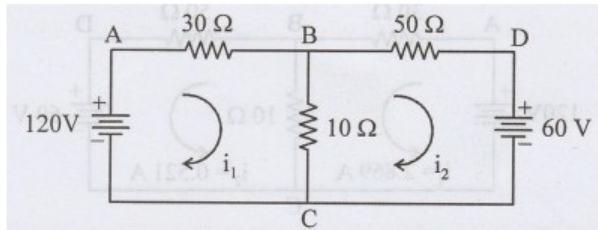21.(a) Determine mesh current I_1, I_2 shown in the figure



Marks	CO	RBT LEVEL
(10)	1	3

(OR)

(b) A coil of resistance 10Ω and inductance 0.1 H is connected in series with a $150 \mu\text{F}$ capacitor across $200\text{V}, 50 \text{ Hz}$ supply. Calculate (i) Inductive reactance, Capacitance reactance, impedance, current and power factor.

(10)	1	3
-------------	----------	----------

22.(a) Explain the principle and construction of D.C. generator with neat diagram.

(10)	2	3
-------------	----------	----------

(OR)

(b) Discuss the working of single phase transformer and derive the emf equation of transformer.

(10)	2	3
-------------	----------	----------

23.(a) Describe the operation of PN junction diode and its characteristics with suitable diagram.

(10)	3	3
-------------	----------	----------

(OR)

(b) Illustrate the input and output characteristics of common emitter .bipolar junction transistor

(10)	3	3
-------------	----------	----------

24.(a) Draw and explain the operation of SR flip-flop with logic diagram.

(10)	4	3
-------------	----------	----------

(OR)

(b) With necessary diagram describe the operation of 4 bit binary asynchronous counter.

(10)	4	3
-------------	----------	----------

25.(a) Illustrate with suitable diagram the construction and working of moving coil type measuring instruments.

(10)	5	2
-------------	----------	----------

(OR)

(b) Describe the construction of induction type energy meter in detail.

(10)	5	2
-------------	----------	----------

PART- C (1x 10=10Marks)

(Q.No.26 is compulsory)

26. The input power to a three phase AC motor is measured as 5 kW . If the voltage and current to the motor are 400 V and 8.6 A respectively. Determine the power factor of the system?

Marks	CO	RBT LEVEL
(10)	1	5
