

Reg. No.

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

B.E. / B.TECH. DEGREE EXAMINATIONS, MAY 2024

First Semester

EE22152 – BASIC ELECTRICAL ENGINEERING

(Electronics and Communication Engineering)

(Regulation 2022)

TIME: 3 HOURS

MAX. MARKS: 100


COURSE OUTCOMES	STATEMENT	RBT LEVEL
CO 1	Analyze DC and AC electrical circuits using Kirchhoff's law.	4
CO 2	Explain the working principle of electrical machines.	4
CO 3	Choose the appropriate electrical machines for various applications.	4
CO 4	To introduce the components of low voltage electrical installations and the working principles of Power converters.	4
CO 5	To study the different types of measuring instruments.	4

PART- A (20 x 2 = 40 Marks)

(Answer all Questions)

1. Estimate the current I_T given $I_1 = -3A$, $I_2 = 6A$, $I_3 = 10A$.


CO	RBT LEVEL
1	2

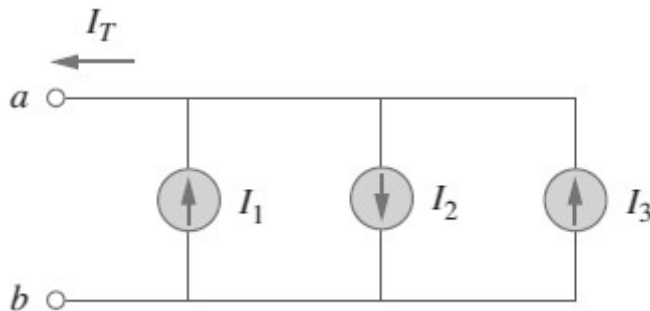

S

2. Solve the given circuit to determine i_x .

CO	RBT LEVEL
1	2

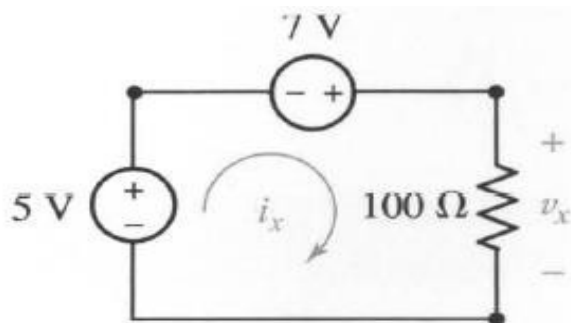


3. Summarize the formulas required for converting star network to delta network.

CO	RBT LEVEL
1	2

4. All resistances in the figure are in ohms.

CO	RBT LEVEL
1	2

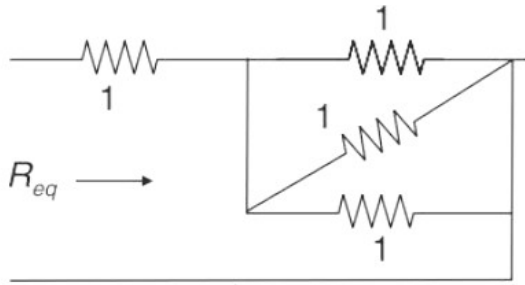
Calculate the value of equivalent resistance R_{eq} .



- | | | | |
|-----|---|---|---|
| 5. | What is back EMF and what is its impact on motor operation. | 2 | 2 |
| 6. | A DC motor has a torque constant K_t of 0.1 Nm/A. If the armature current is 5 A, calculate the torque produced by the motor. | 2 | 2 |
| 7. | Draw the equivalent circuit of a practical transformer. | 2 | 2 |
| 8. | List out the major and minor losses in a transformer. | 2 | 2 |
| 9. | What are the advantages of three phase system over single phase system. | 3 | 2 |
| 10. | How will you find the speed of an ac machine with given frequency and poles? Justify. | 3 | 3 |
| 11. | A 2-pole generator rotor runs at 3600 rpm. Find the electrical frequency of the generated signal. | 3 | 3 |
| 12. | A 12- pole, 50 Hz, three phase induction motor runs at 485rpm. What is the frequency of rotor current? | 3 | 3 |
| 13. | Express the necessity of a fuse in an electrical circuit. | 4 | 3 |
| 14. | Distinguish between MCB and MCCB. | 4 | 2 |
| 15. | Cite the properties of electrical cable. | 4 | 2 |
| 16. | Compute the energy consumption of a system that consumes 190 Watts of power and works for 3 hours a day. | 4 | 3 |
| 17. | Show the figure of a Moving Iron instrument when it is used as a voltmeter and an ammeter. | 5 | 2 |
| 18. | Classify the types of analog meter. | 5 | 2 |
| 19. | Represent the secondary instrument and its types. | 5 | 2 |
| 20. | Indicate the torque is absent in the energy meter. State the reason. | 5 | 3 |


PART- B (5 x 10 = 50 Marks)

- | | Marks | CO | RBT LEVEL |
|---|-------|----|-----------|
| 21. (a) Analyze the circuit to find the mesh currents using Cramer's method and calculate the current through the 8Ω resistor. | (10) | 1 | 4 |

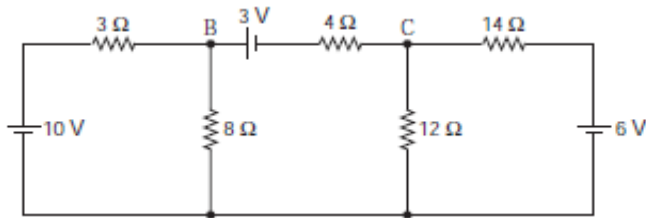

(OR)

(b)

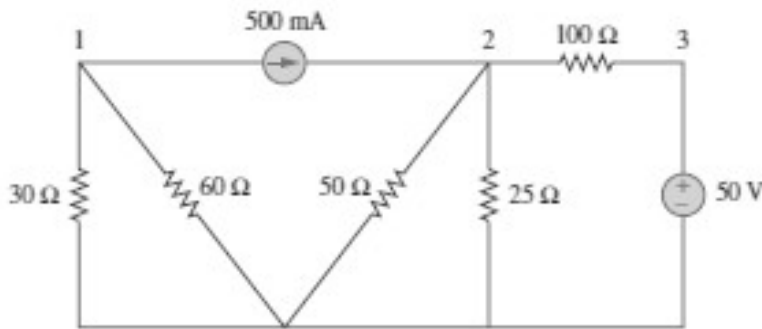

(10) 1 4

Calculate the nodal voltages. Examine the ckt find out node voltages.

22. (a) Draw the circuit of separately excited DC motor. And also explain its construction and working. (10) 2 4

(OR)

(b) Explain the torque- speed characteristics and speed control of separately excited DC motor. (10) 2 4

23. (a) How the RMF is generated in the three-phase induction motor? Explain the construction and working of three phase Induction Motor. (10) 3 4

(OR)

(b) Compare the Induction motor and generator. Also explain the construction and working the synchronous generator? (10) 3 4

24. (a) Construct the buck-boost converter and explain its operation with an equivalent circuit for different modes and waveforms. (10) 4 3

(OR)

(b) Briefly explain the components of LT switchgear and its types. (10) 4 3

25. (a) With the neat sketch, explain the construction and operation of repulsion and attraction type moving iron instruments. (10) 5 4

(OR)

(b) (i) The coil of a measuring instrument has a resistance of 1 Ω, and the (7) 5 4

instrument has a full scale deflection of 250 V when a resistance of 4999 Ω is connected with it. Find the current range of the instrument when used as an ammeter with the coil connected across a shunt of $(1/499) \Omega$ and determine the value of the shunt resistance required for the instrument to display a full scale deflection of 50 A

(ii) Analyze the PMMC instrument with neat diagram. (3) 5 4

PART- C (1 x 10 = 10 Marks)

(Q.No.26 is compulsory)

		Marks	CO	RBT LEVEL
26.	A three -phase 6-pole, 50 Hz induction motor has a slip of 1% at no load and 3% at full load. Find (a)the synchronous speed, (b) the no -load speed, (c) the full- load speed, (d) the frequency of rotor-currents at standstill, and (e)the frequency of rotor-currents at full load.	(10)	2	5
