

Reg. No.

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

B.E./ B.TECH. DEGREE EXAMINATIONS, MAY 2024

Second Semester

EE22201- ELECTRIC CIRCUIT ANALYSIS

(Electrical and Electronics Engineering)

(Regulation 2022)

TIME:3 HOURS


MAX. MARKS: 100

COURSE OUTCOMES	STATEMENT	RBT LEVEL
CO 1	Apply circuit laws to analyze steady-state parameters of given electrical circuits.	4
CO 2	Simplify DC and AC electrical circuits by applying suitable reduction methods and network theorems.	3
CO 3	Analyze three phase balanced and unbalanced circuits to determine power and power factor.	4
CO 4	Analyze transients of electrical circuits and parameters of two-port networks.	4
CO 5	Realize resonance phenomenon and the effect of magnetic coupling in real time applications.	5


PART- A (20x2= 40Marks)

(Answer all Questions)

	CO	RBT LEVEL
1. State Kirchoff's laws.	1	2
2. Give two applications of both series combination and parallel combination.	1	2
3. Find the equivalent impedance across the terminals A-B.	1	2

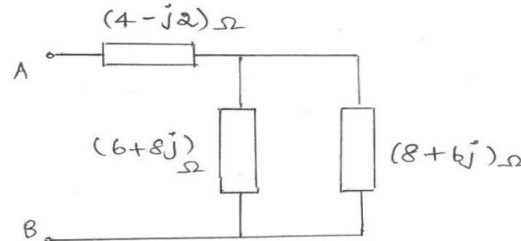


4. Determine the currents I_1 and I_2 in the circuit shown in fig.	1	3
--	---	---

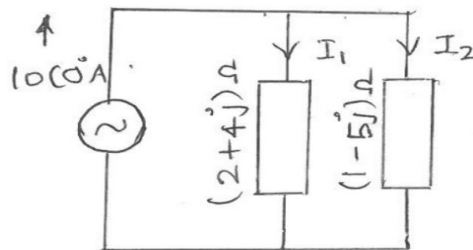

5. State Norton's theorem.	2	2
6. A current $5 \angle -30^\circ$ A is flowing through a circuit consists of series connected when excited by a source of $200 \angle 45^\circ$ V, 50Hz. Analysis the elements of circuit.	2	3
7. The impedance of each branch of a delta connected circuit is $\sqrt{3}Z$. What will be the branch impedance of equivalent star-connected circuit.	2	3

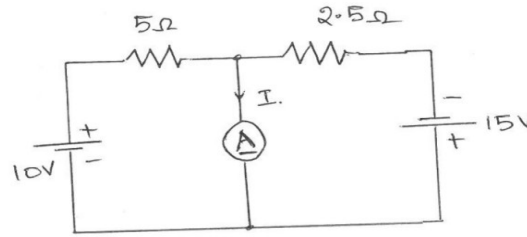
8. Find the current through the ammeter shown in fig. by using super position theorem. 2 3



9. List out the advantages of three phase system over single phase system. 3 2
10. Compare balanced and unbalanced network. 3 2
11. Give the relation connecting the power factor angle with two watt meter readings. 3 2
12. The power input to a three phase induction motor is 20kW when connected to a 3phase, 50Hz,440V supply taking a current of 30A. Calculate the power factor at which motor is working. 3 3
13. Distinguish between steady state and transient state. 4 2
14. What is the time constant of an RC circuit with $R = 10k\Omega$ and $C = 40\mu F$? 4 2
15. What is a two port network and List the various parameter sets that are used to model a two port network. 4 2
16. State the advantages of Laplace transform application to the solution of electric circuit. 4 2
17. Write an expression for the bandwidth of a series resonant circuit in terms of Q factor and the resonant frequency. 5 2
18. Write the characteristics of series resonance. 5 2
19. An RLC series circuit has $R = 10\Omega$ and $X_c = 62.833\Omega$. Find the value of L for resonance at 50Hz. 5 3
20. Write the expression for the equivalent inductance of two coupled coils connected in parallel. 5 2

PART- B (5x 10=50Marks)


- | | Marks | CO | RBT LEVEL |
|---|-------|----|-----------|
| 21.(a) Find the voltage across 5Ω resistor for the circuit shown in fig using Nodal analysis. | (10) | 1 | 4 |

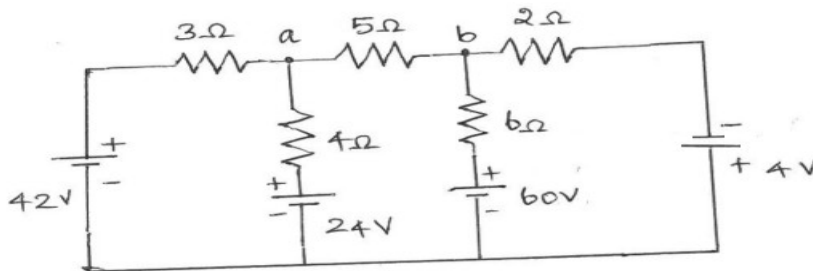


(OR)

- | | | | |
|--|------|---|---|
| (b) Calculate the equivalent impedance of the network across the output terminals A-B shown in fig. If an alternating voltage of $150 \angle 0^\circ$ is connected across A-B. Calculate (i) Total Impedance (ii) The current drawn from the | (10) | 1 | 4 |
|--|------|---|---|

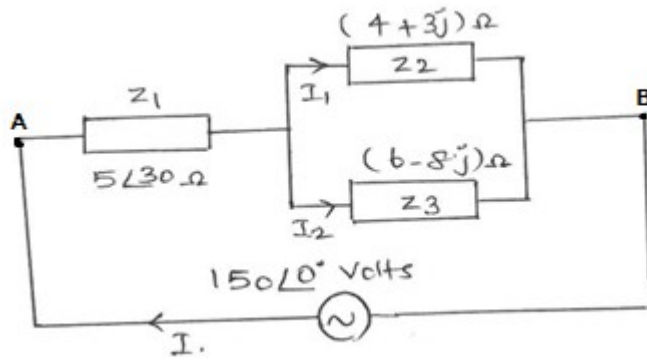source (iii) The current through each impedance (iv) The real power consumed.




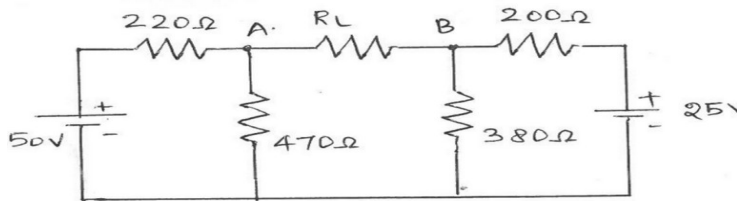- 22.(a) Determine Thevenin's equivalent for the circuit shown in fig. Also, find the optimum value of R_L to derive Maximum power from the network and the Maximum power delivered by R_L . (10) 2 4



(OR)

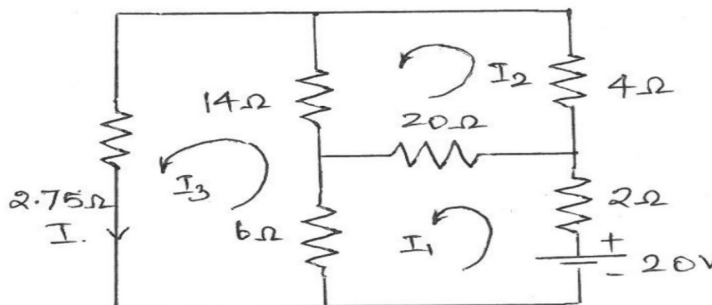- (b) In the shown in figure, Find I_3 and verify the reciprocity theorem. (10) 2 4




- 23.(a) A 3 phase star connected system with 400V (line) is connected to three loads $25 \angle 0^\circ \Omega$, $11 \angle -20^\circ \Omega$ and $15 \angle 16^\circ \Omega$. Find the line current, power and the current in the neutral of the system. (10) 3 4

(OR)

- (b) The two-watt meter produces watt meter readings $W_1=1560W$ and $W_2 = 2100W$ when connected to a delta connected load. If the line voltage is 220V calculate (i) Active Power (ii) Reactive Power (iii) Power factor (iv) Phase Impedance. Is the phase impedance inductive or capacitive? Justify. (10) 3 4

- 24.(a) For the circuit shown in fig, determine the currents $i_1(t)$ and $i_2(t)$ when the switch is closed at $t=0$. Assume that the initial current through the inductor is (10) 4 4

zero.

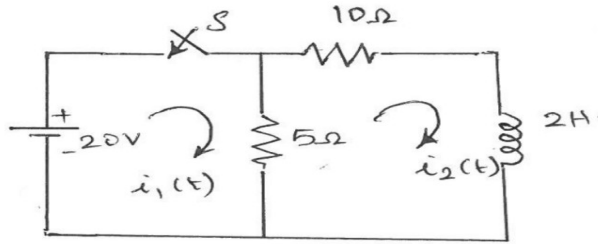

(OR)


(b) Develop an expression for transient current, voltages and the energy stored in capacitor of a RC transient circuit excited by a DC source. (10) 4 4

25.(a) Determine the resonant frequency, bandwidth and quality factor of the coil for the series resonant circuit containing $R=10\Omega$, $L=0.1H$ and $C=10\mu F$. Derive the formula used for bandwidth. (10) 5 4

(OR)

(b) (i) Two coupled coils with $L_1=0.02H$, $L_2=0.01H$ and $K=0.5$ are connected in four different ways, series aiding, series opposing and parallel aiding, parallel opposing. What are the four equivalent inductance? (10) 5 4

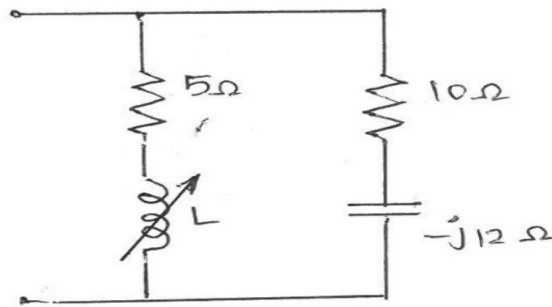(ii) Find the value of L at which the circuit resonates at a frequency of 1000rad/sec in the circuit shown in fig.



PART- C (1x 10=10Marks)

(Q.No.26 is compulsory)

Marks CO RBT LEVEL

26. Use mesh analysis, determine the current through 1Ω , 3Ω , 5Ω resistor for the given circuit. (10) 1 4

