

Reg. No.

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

B.E./ B.TECH. DEGREE EXAMINATIONS, MAY 2024

Third Semester

EE22308 – DIGITAL LOGIC CIRCUITS: THEORY AND PRACTICES*(Electrical and Electronics Engineering)***(Regulation 2022)****TIME:2 HOURS****MAX. MARKS: 60**

COURSE OUTCOMES	STATEMENT	RBT LEVEL
CO 1	Apply the concepts of Boolean algebra and reduction techniques to minimize logic expressions.	3
CO 2	Analyze and design various combinational logic circuits.	4
CO 3	Investigate and design synchronous and asynchronous sequential circuits.	4
CO 4	Comprehend the operation, characteristics of memory devices, digital logic families and construct digital circuits with memory devices.	3
CO 5	Design, debug and verify simple digital circuits and systems with the aid of HDL codes, schematic capture tools and simulation tools.	4

PART- A(10x2=20Marks)

(Answer all Questions)

	CO	RBT LEVEL
1. Convert the octal and hexadecimal equivalent of $(377)_{10}$.	1	2
2. Compare decoder and demultiplexer.	2	2
3. Show the truth table of a simple multiplexer.	2	3
4. Implement full adder logic using 3:8 decoder circuit.	2	3
5. How many flip flops are required to count up to 2024.	2	2
6. Draw the logic diagram of T flip-flop using NAND gates.	2	3
7. Explain briefly Master slave JK flip-flop.	2	2
8. Explain mealy model and Moore model.	3	3
9. Differentiate synchronous and asynchronous sequential circuits.	4	2
10. Compare PROM, PLA and PAL	5	2

PART- B (3x 10=30Marks)

	Marks	CO	RBT LEVEL
11. (a) (i) Simplify the following Boolean function using K-map in SOP form $F(W, X, Y, Z) = \sum(1,3,4,6,9,11,12,14)$. Also Realize the Expression using logic gates.	(5)	1	3

(ii) Encode the binary word 1011 into seven bit even parity Hamming code. (5) 1 3

(OR)

(b) Design and implement the simplest circuit that has three inputs, X_1 , X_2 , and X_3 , which produces an output value of 1 whenever exactly one or two of the input variables have the value 1; otherwise, the output has to be 0. (10) 1 3

12. (a) A sequential circuit with two D flip-flops A and B; input X and output Y is specified by the following next state and output equations: (10) 3 4

$$A_+ = AX + BX; B_+ = A'X \text{ and } Y = (A+B) X'$$

Derive the state table and state diagram. Also draw the logic diagram of the circuit.

(OR)

(b) Design and analyze a 4-bit ring counter and mention its applications. (10) 3 4

13. (a) Design a Asynchronous decade counter. (10) 4 4

(OR)

(b) (i) What are static-0 and static-1 hazards? Show the removal of hazards using hazard covers in K-map. (5) 4 4

(ii) Examine cycles and races in asynchronous sequential circuits. (5) 4 4

PART- C (1x 10=10Marks)

(Q.No.14 is compulsory)

		Marks	CO	RBT LEVEL
14.	Implement the combinational circuit with a PLA having 3 inputs, 4 product terms and 2 outputs for the functions. $F_1(A, B, C) = \sum (0, 1, 2, 4)$ $F_2(A,B,C)=\sum(0,5,6, 7)$	(10)	5	5
