

Reg. No.

| | | | | | | | | | | | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|
| | | | | | | | | | | | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|

B.E./ B. TECH.DEGREE EXAMINATIONS, MAY 2024

Third Semester

EE22309– ELECTRON DEVICES AND CIRCUITS: THEORY AND PRACTICES*(Electrical and Electronics Engineering)***(Regulation 2022)****TIME:2 HOURS****MAX. MARKS: 60**

| COURSE OUTCOMES | STATEMENT | RBT LEVEL |
|-----------------|--|-----------|
| CO 1 | Apply the concepts of PN junction devices and analyse its various electronic circuits | 4 |
| CO 2 | Analyse the various configurations of bipolar junction transistors and amplifiers. | 4 |
| CO 3 | Analyse the various configurations of field effect transistors and amplifiers. | 4 |
| CO 4 | Analyse the performance of multistage and feedback amplifier circuits. | 4 |
| CO 5 | Understand the operation of oscillators and Optoelectronic devices and analyse its behaviour | 4 |

PART- A(10x2=20Marks)

(Answer all Questions)

| | CO | RBT LEVEL |
|---|----|-----------|
| 1. The reverse saturation current of a silicon pn junction diode is $10\mu\text{A}$. Calculate the diode current for the forward bias voltage of 0.7V at 25°C . | 1 | 3 |
| 2. Give the effect of Temperature on PN Junction diode. | 1 | 2 |
| 3. Which of the BJT configuration is suitable for impedance matching application? Why? | 2 | 3 |
| 4. When the drain voltage increases beyond the pinch off voltage, What will happen to the drain current? | 3 | 2 |
| 5. The data sheet of JFET indicates that it has $I_{DSS}=14\text{mA}$ and $V_{GS}(\text{off})=-5\text{V}$. Calculate the value of I_D when V_{GS} is (i) 0V and (ii) -5V . | 3 | 3 |
| 6. Which MOSFET is called as normally ON MOSFET? Why? | 3 | 2 |
| 7. How to protect the MOSFET from stray voltages? | 3 | 2 |
| 8. Draw the equivalent circuit of UJT. | 3 | 2 |
| 9. Single stage amplification is not sufficient to meet the power requirement in particular application, Mention the method to meet the power requirement? | 4 | 3 |
| 10. Mention the application of Photodiode and phototransistor. | 5 | 2 |

PART- B (3x 10=30Marks)

| | Marks | CO | RBT LEVEL |
|---|-------|----|-----------|
| 11. (a) (i) With the necessary diagrams, analyze forward and reverse characteristics of PN diode. | (5) | 1 | 3 |

(ii) Derive the expression for diffusion capacitance in PN diode.

(5) 1 3

(OR)

(b) In an application which needs the output voltage to be regulated. Choose the appropriate device, that would ensure this operation with appropriate circuit. Also discuss how it regulates the voltage.

(10) 1 3


12. (a) Design a Voltage divider bias circuit for transistor to establish the quiescent point as $V_{CE}=12V$, $I_C=1.5mA$, stability factor $S \leq 3$, $\beta=50$, $V_{BE}=0.7V$, $V_{CC}=22.5V$, $R_C=5.6K\Omega$.

(10) 2 4

(OR)

(b) Using the small signal model, Derive the expression for voltage gain, input and output impedance of the figure shown below.

(10) 2 4

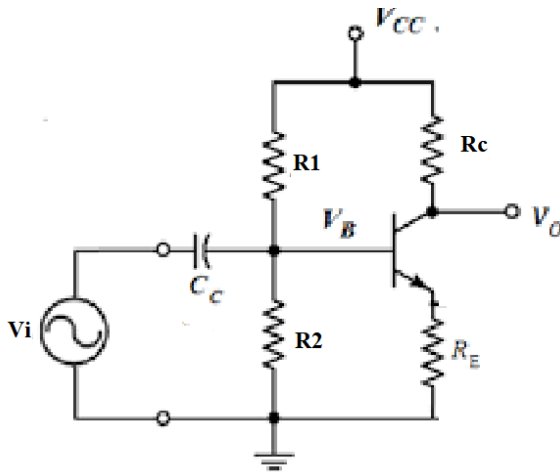

13. (a) Discuss the principle and operation of a Colpitts oscillator and also derive the frequency of oscillations.

(10) 5 3

(OR)

(b) Design an oscillator to operate at a frequency of 1KHz which gives an extremely pure sine wave output and good frequency stability. Discuss the operation of this oscillator as an audio signal generators.

(10) 5 3

PART- C(1x 10=10Marks)

(Q.No.14 is compulsory)

14. Identify the feedback topology used in emitter follower circuit. With the help of h parameter equivalent circuit, derive the expression for voltage gain, input impedance and output impedance.

| Marks | CO | RBT LEVEL |
|-------|----|-----------|
| (10) | 4 | 4 |
